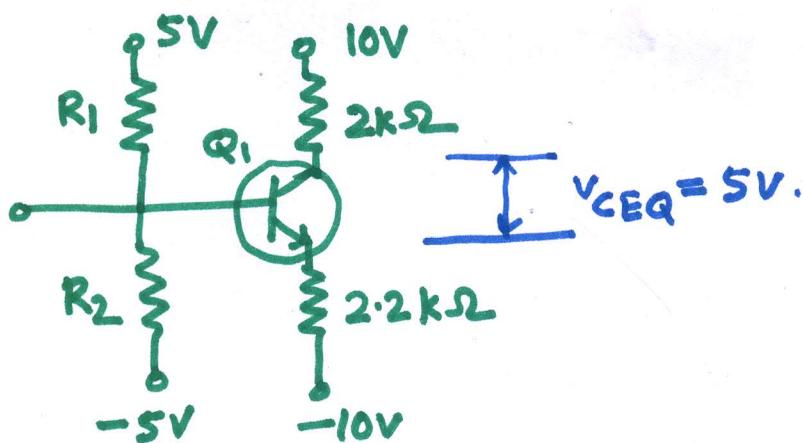


Solutions of Quiz - II

Basic ECE Q.

RAKTIM HALDAR.

Q.1.



for stability.

$$R_{TH} = \frac{1}{10}(1+\beta)R_E \\ = 13.42 \text{ k}\Omega$$

Options (b), (c), (d)
satisfy this.
Eliminate (a).


Now, find I_E, I_c .

$$\text{from KVL} \rightarrow 10 - 2I_c - 5 - 2.2I_E - (-10) = 0$$

$$\Rightarrow 10 - 2\beta I_B - 5 - 2.2(1+\beta)I_B + 10 = 0 .$$

$$\therefore I_B = 0.06 \text{ mA.}$$

I/P Loop:

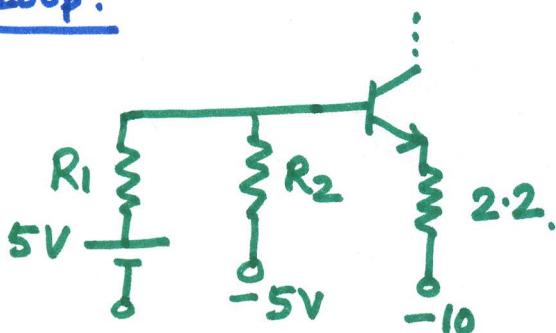

$$V_{TH} = \frac{10R_2}{R_1+R_2} - 5$$

$$R_{TH} = 13.42 \text{ k}\Omega = \frac{R_1R_2}{R_1+R_2}$$

$$\text{Now, } I_B = \frac{V_{TH} - 0.7 - (-10)}{R_{TH} + (1+\beta)R_E} = 0.06$$

$$\therefore V_{TH} = -0.4428.$$

$$\therefore \frac{10R_2}{R_1+R_2} = 0.4428 + 5 = 4.5572V$$

$$\therefore \frac{10R_2}{R_1+R_2} = 4.5572. \quad \textcircled{I} \quad \frac{R_1R_2}{R_1+R_2} = 13.42 \quad \textcircled{II}$$

Dividing $\textcircled{I}/\textcircled{II} \rightarrow$


$$\frac{10R_2}{R_1+R_2} \times \frac{R_1+R_2}{R_1R_2} = 0.3388$$

$$\therefore R_1 \approx 29.45. k\Omega$$

$$R_2 \approx 29.66 k\Omega.$$

[Ans. (c)]

Q.2.

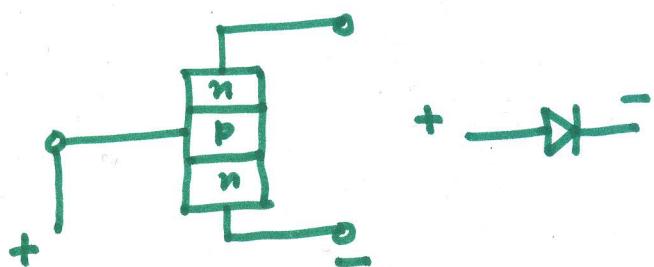

forward bias.
Low resistance.

Ans. (c)

Q.3.

$$V_{TH} = \frac{20R_2}{R_1+R_2} = 3.7V, \quad R_{TH} = 4.074 k\Omega.$$

$$\therefore I_B = \frac{V_{TH} - 0.7}{R_{TH} + (1+\beta)R_E} = 0.05497 mA \approx 0.06 mA$$

$$\therefore I_E = (1+\beta)I_B = 5.55 mA \approx 6 mA.$$


Ans: (d)

4.  $\hat{A} = \text{OPAMP} \rightarrow \text{vCVS}$ (Ans: (a))
 Voltage \xrightarrow{G} Voltage
 $G \rightarrow \text{HIGH Gain.}$

5. $G = \left(1 + \frac{R_2}{R_1}\right) > 1$ (b) Greater than one.

6. (d) Inverting

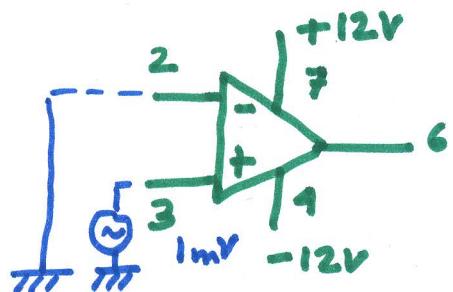7. This one is nearly a tricky and beautiful Q.




The gain (open-loop) is very high. ideally $\rightarrow \infty$

But the dc bias provides maximum of 12V. So the o/p cannot be more than

this (ofcourse not infinite). The OPAMP will saturate before this.

So,

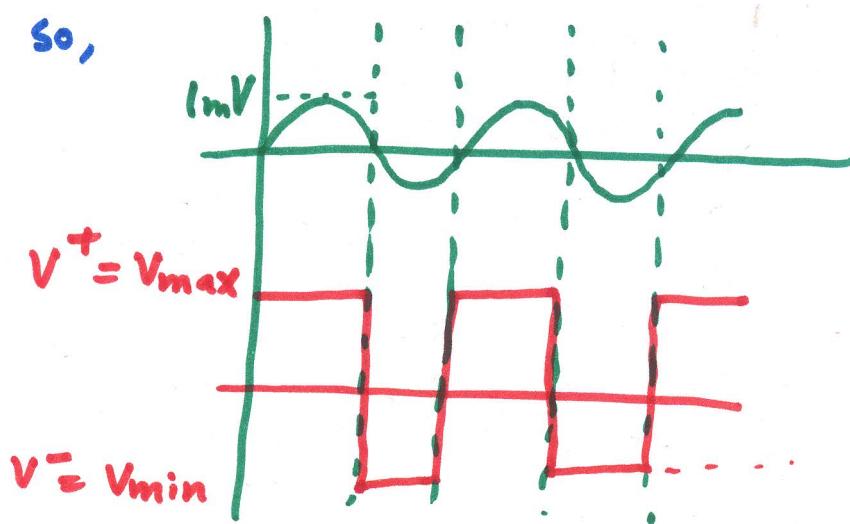

← Applied to the non-inverting terminal (+)
 So, —

Ans. (b) square wave

8. Read OPAMP frequency response.

The gain-bandwidth product for an OPAMP will be constant.

$$\therefore G \times BW = C$$

$$\therefore I \times 1.5 \times 10^6 = 100,000 \times f_c$$

$$\therefore f_c = 15 \text{ Hz.}$$

Ans. (c) 15 Hz.


9.

$$CMRR = 20 \log_{10} \frac{A_d}{A_{CM}} = 90.$$

Ans: (d)

$$A_d = 150$$
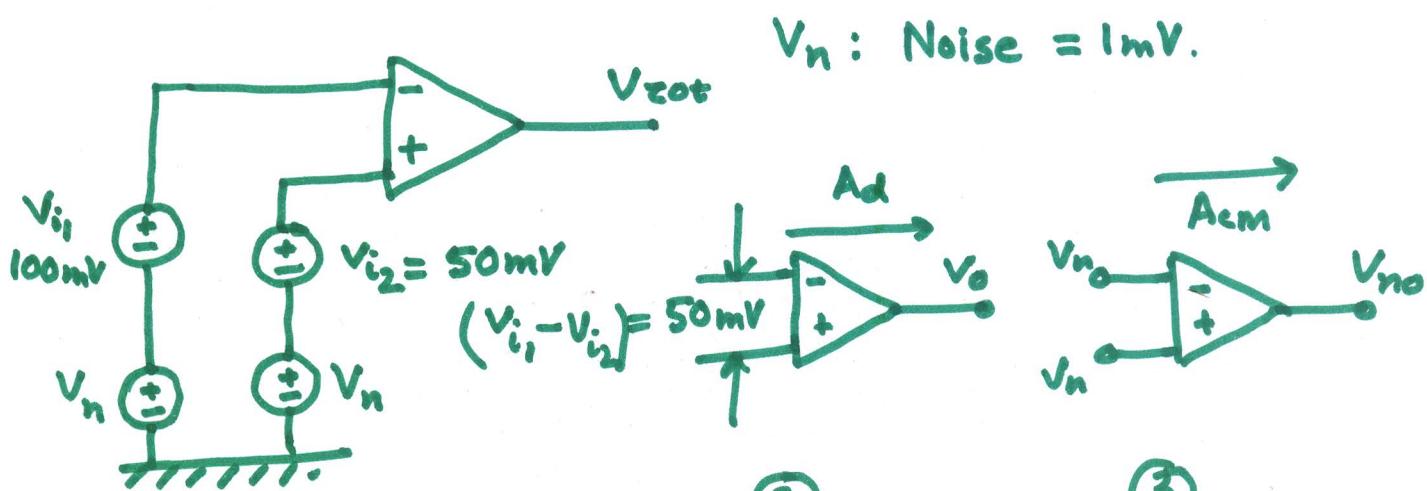
$$\therefore A_{CM} \approx 9.7 \times 10^{-3}.$$



① Total

② Differential


③ Common mode

$$\therefore \text{Differential Voltage} = V_{i1} - V_{i2} = V_d = 50 \text{ mV.}$$

$$\therefore \text{O/P Signal} = V_o = A_d V_d = 150 \times 50 = \underline{\underline{7.5 \text{ V}}} \quad \text{I}$$

$$\text{Common Voltage} = \text{Noise} = V_n = 1 \text{ mV.}$$
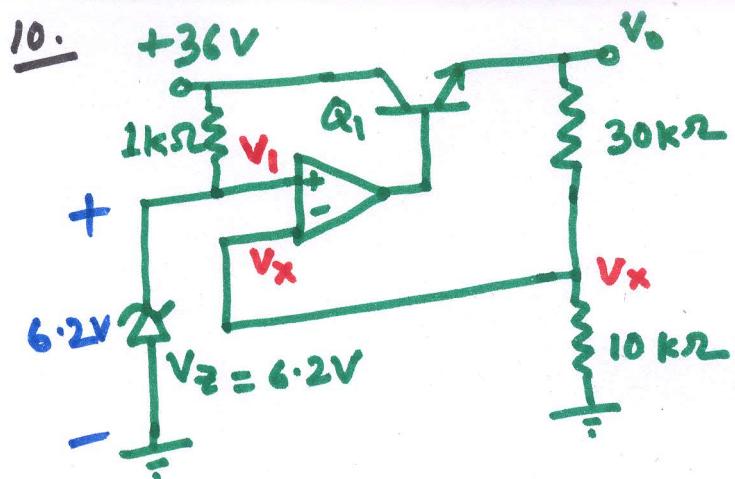
$$\therefore \text{O/P Noise} = V_{no} = A_{CM} \cdot V_n = \underline{\underline{9.7 \times 10^{-6} \text{ V.}}} \quad \text{II}$$



$$V_1 = 6.2 \text{ V}$$

One can check that the Zener diode would be ON by open-circuit the Zener diode.

So, if the OPAMP is ideal.

$$V_x \approx V_1 = 6.2 \text{ V}.$$


$$\therefore V_x = \frac{V_o \times 10}{30+10} \text{ (voltage divider).}$$

$$\therefore V_o = 6.2 \times 4 = 24.8 \text{ V.}$$

[Ans. (b)]

II. One can guess the ans will be 24.7V

procedure →

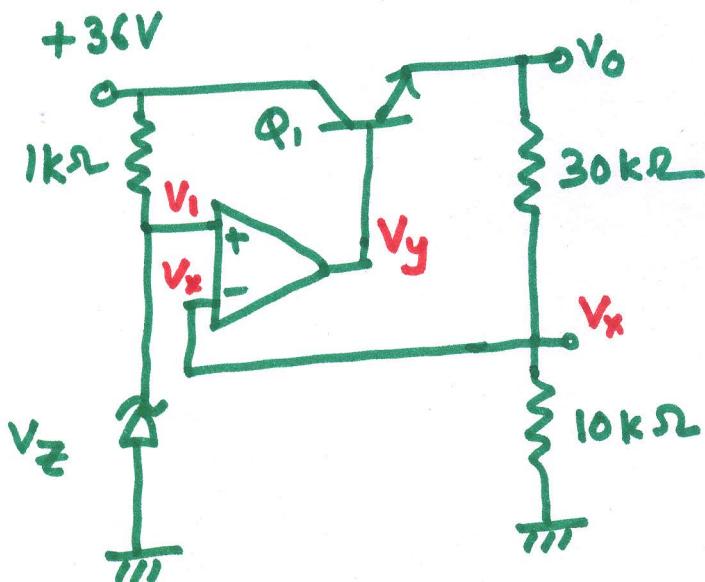

$$V_1 = 6.2 \text{ V}$$

$V_x \neq V_1$ (as the OPAMP is not ideal now).

Rather,

$$V_y = (V_1 - V_x) \times 1000.$$

$$\text{now, } V_o = (V_y - 0.7 \text{ V})$$

$$\text{again } V_x = \frac{V_o \times 10}{40}$$


$$\therefore V_o = 4V_x.$$

$$\therefore (V_1 - V_x) \times 1000 - 0.7 = V_o = 4V_x.$$

Solve this, you will eventually get, V_x, V_o both.

Ans: (a) 24.7V

13.

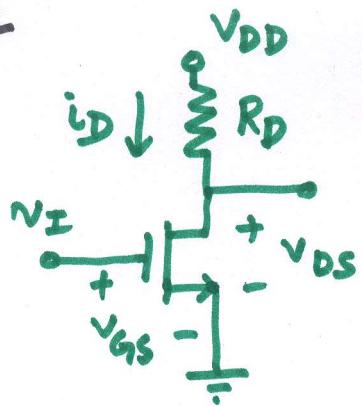

The MOSFET is biased in the non-saturation region.

$$i_D = k_n [2(v_I - v_{TN})v_o - v_o^2]$$

$$v_o = v_{DD} - i_D R_D.$$


$$P = v_o \times i_D$$

$$\therefore v_o = 0.2V, v_I = 5V, v_{TN} = 1V, R_D = 500\Omega.$$

$$\therefore k_n = 6.15 \text{ mA/V}^2 \text{ and } P = 1.92 \text{ mW}$$

Ans: (b) 1.92 mW.

14.

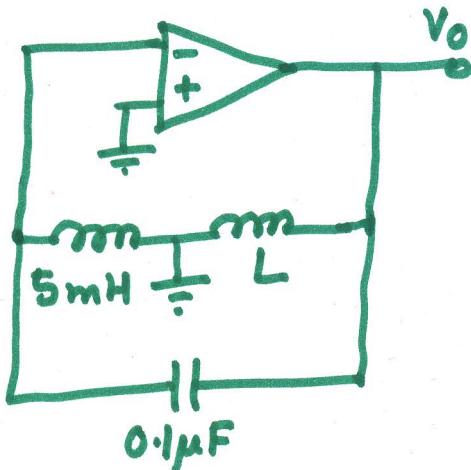

$$f = \frac{1}{2\pi \sqrt{L_{eq} C}}$$

$$L_{eq} = \frac{1}{4\pi^2 f^2 C} = 101 \text{ mH.}$$

$$L_{eq} = L + 5 \text{ mH.}$$

$$\therefore L \approx 96 \text{ mH.} \approx 96.3 \text{ mH}$$


Ans: (C) 96.3 mH.

This is probably the configuration with OPAMP. Please confirm if it is included in the syllabus or not.

'Hartley Oscillator'

15.

□ Gate as a switch: Controlled switch

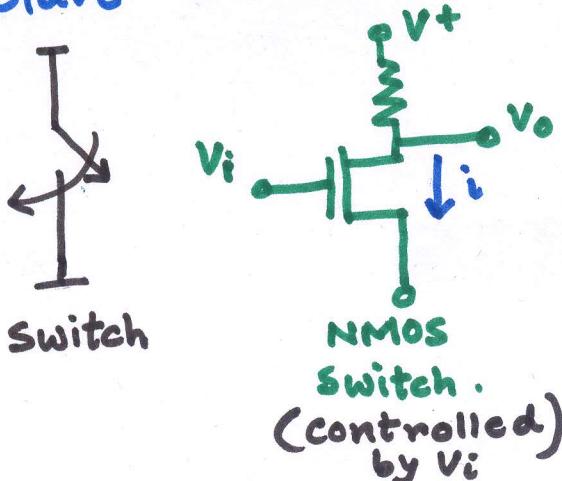




1. If $V_i = 5V$ (ON)/HIGH (logical 1)
2. then current will flow through NMOS
3. So, NMOS \rightarrow ON or short-circuited with GND.

∴ So, if $V_i = 1$ (5V) \rightarrow NMOS ON \rightarrow SHORT with Ground, $\rightarrow V_o = 0$ (0V)

5. NMOS \rightarrow NOT GATE.

So, for this problem,—

If Both $A, B = 1$ then $V_o = 0$

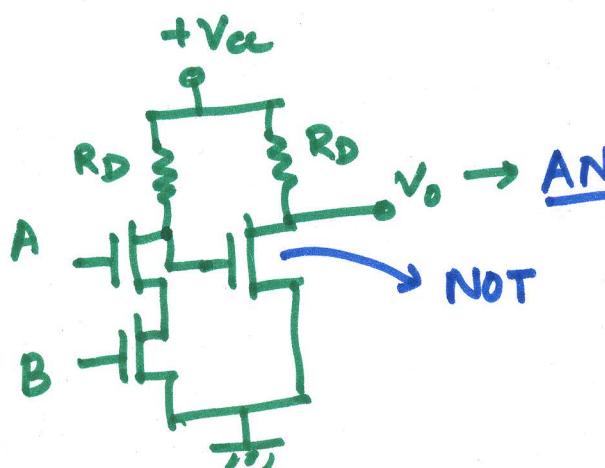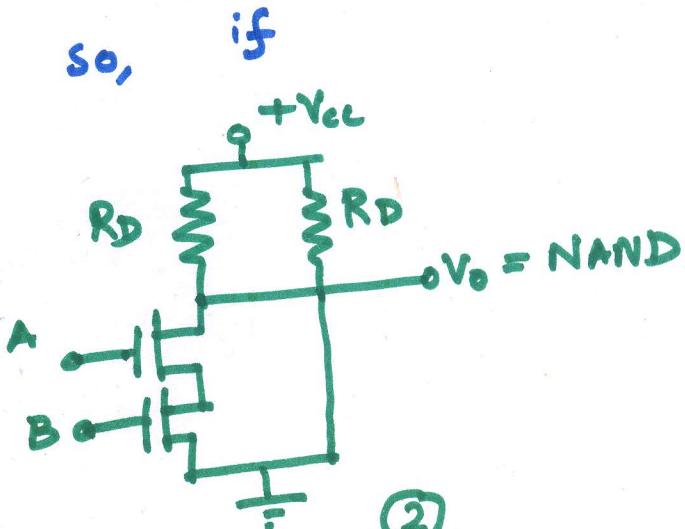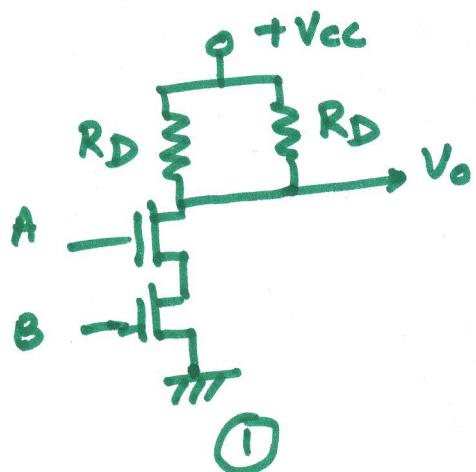

(Extra NOT is there)
 \therefore NAND + NOT = AND.

Ans: (a) AND.