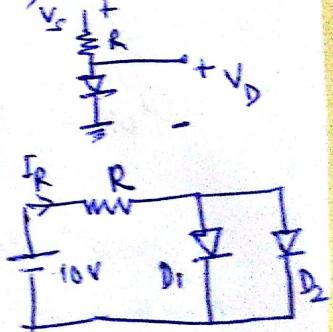


- Q1 (a) An abrupt Si p-n junction node has
- 11 - 1
- $N_A = 10^{23}/m^3$  on p-side  
 $N_D = 10^{21}/m^3$  on n-side
- (i) Calculate the majority & minority concn for both side  
(ii) Calculate the contact potn & the width of the depletion region under zero bias condn. at 300 K  
assume the intrinsic carrier concn of Si is  $1.5 \times 10^{16}/m^3$  &  $E_F = 11.8$

Q2. The bandgap of  $\text{GaAs}$  and  $\text{Al}_x\text{As}$  are  $1.43 \text{ eV}$  and  $2.16 \text{ eV}$  resp. Assuming the bandgap of  $\text{Al}_x\text{Ga}_{1-x}\text{As}$  to vary linearly with  $x$  b/w the two extreme values ( $0, 1$ ), find the value of  $x$  that would ~~not~~ result in the emission of  $600 \text{ nm}$  from  $\text{Al}_x\text{Ga}_{1-x}\text{As}$

- (Q2) (a) Consider the circuit shown in Fig 1,  $R = 10\text{k}\Omega$ ,  $V_S^+$  consists of a dc value of 10V which is superimposed with a ac voltage of 1-V peak amplitude & 60 Hz frequency.  
 Calculate both the dc & ac voltage across the diode, Assume the diode is of  $\text{Si}$ -type
- (b) In the circuit of Fig. 2,  $V_{T_1} = 0.6\text{V}$  and  $V_{T_2} = 0.3\text{V}$   
 calculate the  $I_R$ ,  $R = 330\Omega$



③

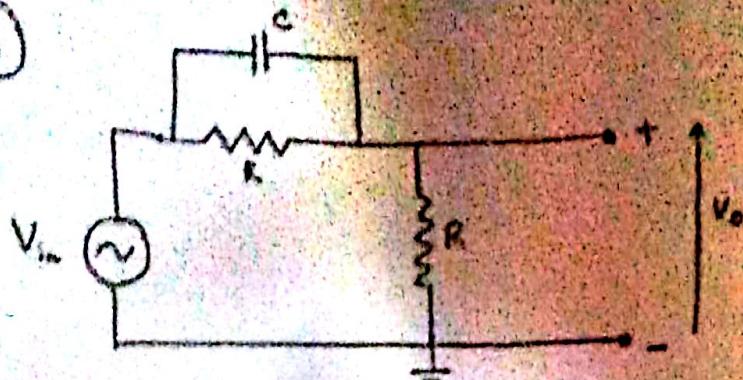



Fig.3

For the circuit shown in Fig. 3. Obtain the complex transfer function and express them in magnitude and phase form, for  $R = 1k\Omega$ ,  $C = 1\mu F$ , Calculate the 3-dB cut-off frequency and the frequency at which the phase difference between input and output voltage is  $45^\circ$ .

④

Identify each of these filter types and explain how you were able to identify their characteristics.

a)

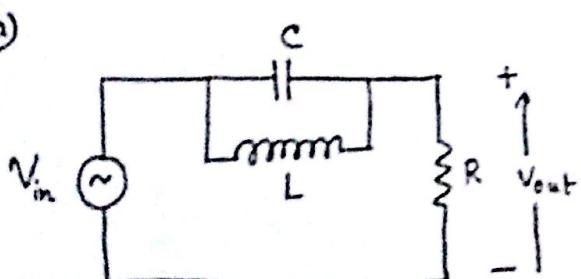

b)

